

# NASA TECH BRIEF



NASA Tech Briefs are issued to summarize specific innovations derived from the U. S. space program and to encourage their commercial application. Copies are available to the public from the Clearinghouse for Federal Scientific and Technical Information, Springfield, Virginia 22151.

## Bipolar Current Driver for Memory Circuits

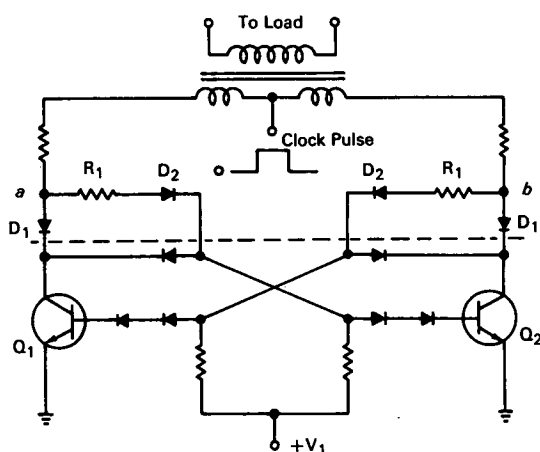


FIGURE 1

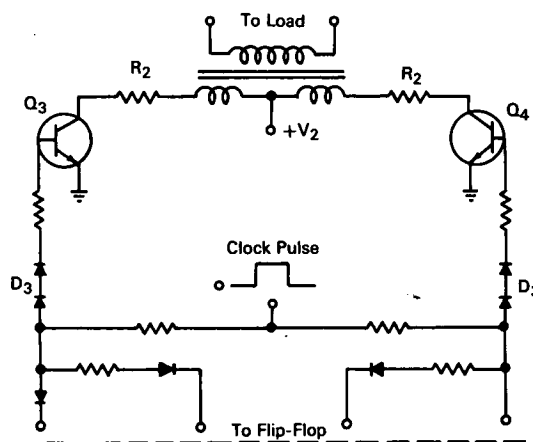


FIGURE 2

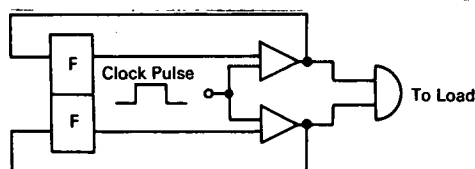


FIGURE 3

### The problem:

To provide a bipolar driving current to a memory circuit, the polarity of which is determined by the state of a flip-flop. Ordinarily, the current flowing in the flip-flop is insufficient to act as a driving current since the logic circuit operates at a much lower level than is required for the driving circuit.

### The solution:

A circuit which logically determines the state of a flip-flop and amplifies the current from a clock pulse flowing through the flip-flop by means of a feedback mechanism.

### How it's done:

The circuit to be "read" is a standard low-current flip-flop, the portion below the dashed line in figure 1. Assume that  $Q_1$  is conducting while  $Q_2$  is nonconducting. With the clock pulse at ground potential, diodes  $D_1$  and  $D_2$  are back-biased and no current flows in the bit driver network (above the dashed line in figure 1). When a positive clock pulse is applied, the potential at node  $b$  increases far more than the potential at node  $a$  because transistor  $Q_1$  remains in saturation. The potential at node  $b$  increases the forward bias of  $Q_1$ , allowing it to pass the additional current. Transistor  $Q_2$  remains nonconducting since

(continued overleaf)

the small voltage at node  $a$  is insufficient to forward bias  $Q_2$  in view of  $R_1$  and the three diodes in the base connection. The current flowing from the clock pulse is transformer coupled to the load, and if  $Q_2$  instead of  $Q_1$  were conducting, a current of opposite polarity would be passed to the load. Thus the clock pulse supplies load current and steps up the operating level of the flip-flop. This circuit will provide sufficient driving current to the load if the clock pulse is of sufficient amplitude, and if the flip-flop is able to handle the additional current.

In cases in which the ratio of required load current to normal flip-flop current is very high (on the order of  $10^4$ ), a circuit such as that in figure 2 may be used. This circuit logically determines the state of the flip-flop as previously, but provides additional amplification through transistor  $Q_3$  or  $Q_4$ . The resistors  $R_2$  determine the collector current of the transistors, and diodes  $D_3$  insure that either  $Q_3$  or  $Q_4$  will remain off.

Figure 3 illustrates the logic of operation of the circuits. The output of the "high" or "on" side of the flip-flop is amplified when the clock pulse is applied. Part of the amplified output is then fed back to the input of the flip-flop, thus increasing gain. The two outputs of the amplifiers are then appropriately connected to the load through transformer coupling.

#### Notes:

1. This principle may be applied to various memory driving circuits where power dissipation must be minimized.
2. One of the advantages of the type of driver illustrated in figure 1 is that fast rise times and short delays are obtained with ease because auxiliary amplifying components are not used.
3. Inquiries concerning this invention may be directed to:

Technology Utilization Officer  
Goddard Space Flight Center  
Greenbelt, Maryland 20771  
Reference: B66-10469

#### Patent status:

Inquiries about obtaining rights for the commercial use of this invention may be made to NASA, Code GP, Washington, D.C. 20546.

Source: C. F. Chong and C. A. Nelson  
of Sperry Rand Corporation  
under contract to  
Goddard Space Flight Center  
(GSFC-213)